

MASSACHUSETTS INSTITUTE OF TECHNOLOGY
DEPARTMENT OF ELECTRICAL ENGINEERING AND COMPUTER SCIENCE

6.004 Computation Structures

Lab #1

General Information

Lab assignments are due on Thursdays; check the on-line course calendar for the actual due date for each lab. Look at the on-line questions before you start to see what information you should collect while working on each lab. The on-line questions can be loaded from the “On-line assignments” page accessible from the navigation sidebar on the course website (<http://6004.mit.edu>). If you have difficulties, questions or suggestions with the on-line system please post a question/comment to Piazza (follow link on course website)..

You can visit each on-line question page as many times as necessary to complete the assignment – you do not have to answer all the questions in a single session. Click on the “Save” button at the bottom of the question page to save your answers. You can then come back to the page later on and pick up where you left off. You can also check your answers at any time by clicking on the “Check” button. When the system detects that all your answers are correct (either because of a “Check” or “Save”), it will give you credit for completing the assignment.

To receive credit for a lab, you’ll need to have a short **lab checkoff meeting** with a member of the course staff and answer some questions about your work. Just come by the lab after you’ve completed your check-in and talk with one of the on-duty staff. The meeting can happen after the due date of the lab but to receive full credit you must **complete the meeting within one week of the lab due date**. To avoid long waits choose a time other than Wednesday or Thursday evenings.

The lab gets crowded just before an assignment is due and some of the problems are too long to be done the night before the due date, so plan accordingly. There will be course staff in the lab during the late afternoon and evening; check the course website for this semester’s schedule.

The 6.004 lab is located in 32-083 and is open 24 hours-a-day, 7 days-a-week. An access code is required for entry; it was given out in the email that included your section assignment. The lab has Linux-Athena workstations that can be used to complete the homework assignments. The lab software is written in Java and should run on any Java Virtual Machine supporting JDK 1.3 or higher. The courseware can be run on any Linux-Athena workstation. You can also download the courseware for your Linux, Windows, or Macintosh computer – see the “Courseware” page on the 6.004 website.

1: Introduction to JSim

In this lab, we'll be using a *simulation program* (JSim) to make some measurements of an N-channel mosfet (or “nfet” for short). JSim uses mathematical models of circuit elements to make predictions of how a circuit will behave both statically (DC analysis) and dynamically (transient analysis). The model for each circuit element is parameterized, e.g., the mosfet model includes parameters for the length and width of the mosfet as well as many parameters characterizing the physical aspects of the manufacturing process. For the models we are using, the manufacturing parameters have been derived from measurements taken at the integrated circuit fabrication facility and so the resulting predictions are quite accurate.

The (increasingly) complete JSim documentation can be found at the course website. But we'll try to include pertinent JSim info in each lab writeup.

To run JSim, login to an Athena console. We recommend using the computers in the 6.004 lab (32-083) since JSim has been tested and is known to run with satisfactory performance in that environment. Another benefit of using the 6.004 lab is that there's plenty of help around, both from your fellow students and the course staff. After signing onto the Athena station, add the 6.004 locker to gain access to the design tools and model files (you only have to do this once each session):

```
athena% add 6.004
```

Start JSim running in a separate window by typing

```
athena% jsim &
```

It can take a few moments for the Java runtime system to start up, please be patient! JSim takes as input a *netlist* that describes the circuit to be simulated. The initial JSim window is a very simple editor that lets you enter and modify your netlist. You may find the editor unsatisfactory for large tasks—it's based on the JTextArea widget of the Java Swing toolkit that in some implementations has only rudimentary editing capabilities. If you use a separate editor to create your netlists, you can have JSim load your netlist files when it starts:

```
athena% jsim filename ... filename &
```

Two limitations of the JSim editor are that **Ctrl-S does not save** and **there is no undo**.

1: Introduction to JSim

There are various handy buttons on the JSim toolbar:



Exit. Asks if you want to save any modified file buffers and then exits JSim.



New file. Create a new edit buffer called “untitled”. Any attempts to save this buffer will prompt the user for a filename.



Open file. Prompts the user for a filename and then opens that file in its own edit buffer. If the file has already been read into a buffer, the buffer will be reloaded from the file (after asking permission if the buffer has been modified).



Close file. Closes the current edit buffer after asking permission if the buffer has been modified.



Reload file. Reload the current buffer from its source file after asking permission if the buffer has been modified. This button is useful if you are using an external editor to modify the netlist and simply want to reload a new version for simulation.



Save file. If any changes have been made, write the current buffer back to its source file (prompting for a file name if this is an untitled buffer created with the “new file” command). If the save was successful, the old version of the file is saved with a “.bak” extension.



Save file, specifying new file name. Like “Save file” but prompts for a new file name to use.



Save all files. Like “save file” but applied to all edit buffers.



Stop simulation. Clicking this control will stop a running simulation and display whatever waveform information is available.



Device-level simulation. Use a Spice-like circuit analysis algorithm to predict the behavior of the circuit described by the current netlist. After checking the netlist for errors, JSim will create a simulation network and then perform the requested analysis (i.e., the analysis you asked for with a “.dc” or “.tran” control statement). When the simulation is complete the waveform window is brought to the front so that the user can browse any results plotted by any “.plot” control statements.



Fast transient analysis. This simulation algorithm uses more approximate device models and solution techniques than the device-level simulator but should be

much faster for large designs. For digital logic, the estimated logic delays are usually within 10% of the predictions of device-level simulation. This simulator only performs transient analysis.



Gate-level simulation. This simulation algorithm only knows about gates and logic values (instead of devices and voltages). We'll use this feature later in the term when trying to simulate designs that contain too many mosfets to be simulated at the device level.



Switch to waveform window. In the waveform window this button switches to the editor window. Of course, you can accomplish the same thing by clicking on the border of the window you want in front, but sometimes using this button is less work.



Using information supplied in the checkoff file, check for specified node values at given times. If all the checks are successful, submit the circuit to the on-line assignment system.

The waveform window shows various waveforms in one or more “channels.” Initially one channel is displayed for each “.plot” control statement in your netlist. If more than one waveform is assigned to a channel, the plots are overlaid on top of each using a different drawing color for each waveform. If you want to add a waveform to a channel simply type the appropriate signal name in the list appearing to the left of the waveform display (the name of each signal should be on a separate line). You can also add the name of the signal you would like displayed to the appropriate “.plot” statement in your netlist and rerun the simulation. If you simply name a node in your circuit, its voltage is plotted. You can also ask for the current through a voltage source by entering “I(Vid)”.

The waveform window has several other buttons on its toolbar:



Select the number of displayed channels; choices range between 1 and 16.



Print. Prints the contents of the waveform window (in color if you have a color printer!). If you are using Athena, you have to print to a file and then send the file to the printer: select "file" in the print dialog, supply the name you'd like to use for the plot file, then click "print". You can send the file to one of the printers in the lab using "lpr", e.g., "lpr -Pcs foo.plot".

You can zoom and pan over the traces in the waveform window using the control found along the bottom edge of the waveform display:



zoom in. Increases the magnification of the waveform display. You can zoom in around a particular point in a waveform by placing the cursor at the point on the trace where you want to zoom in and typing upper-case “X”.

1: Introduction to JSim



zoom out. Decreases the magnification of the waveform display. You can zoom out around a particular point in a waveform by placing the cursor at the point on the trace where you want to zoom out and typing lower-case “x”.



surround. Sets the magnification so that the entire waveform will be visible in the waveform window.

The scrollbar at the bottom of the waveform window can be used to scroll through the waveforms. The scrollbar will be disabled if the entire waveform is visible in the window. You can recenter the waveform display about a particular point by placing the cursor at the point which you want to be at the center of the display and typing “c”.

The JSim netlist format is quite similar to that used by Spice, a well-known circuit simulator. Each line of the netlist is one of the following:

A *comment line*, indicated by an “*” (asterisk) as the first character. Comment lines (and also blank lines) are ignored when JSim processes your netlist. You can also add comments at the end of a line by preceding the comment with the characters “/” (C++- or Java-style comments). All characters starting with “/” to the end of the line are ignored. Any portion of a line or lines can be turned into a comment by enclosing the text in “/*” and “*/” (C-style comments).

A *continuation line*, indicated by a “+” (plus) as the first character. Continuation lines are treated as if they had been typed at the end of the previous line (without the “+” of course). There’s no limitation on the length of an input line but sometimes it’s easier to edit long lines if you use continuation lines. Note that “+” also continues “*” comment lines!

A *control statement*, indicated by a “.” (period) as the first character. Control statements provide information about how the circuit is to be simulated. We’ll describe the syntax of the different control statements as we use them below.


A *circuit element*, indicated by a letter as the first character. The first letter indicates the type of circuit element, e.g., “r” for resistor, “c” for capacitor, “m” for mosfet, “v” for voltage source. The remainder of the line specifies which circuit nodes connect to which device terminals and any parameters needed by that circuit element. For example the following line describes a 1000 Ω resistor called “R1” that connects to nodes A and B.

```
R1 A B 1k
```

Note that numbers can be entered using engineering suffixes for readability. Common suffixes are “k”=1000, “u”=1E-6, “n”=1E-9 and “p”=1E-12.

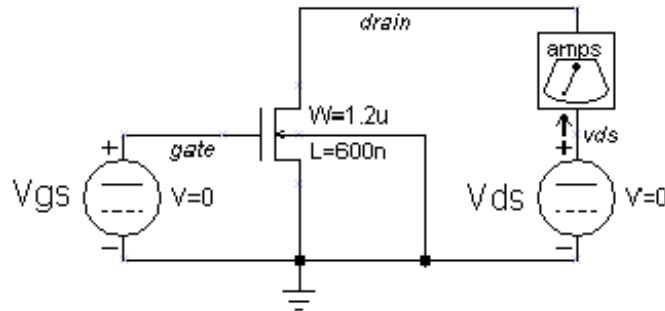2: Characterizing MOSFETs

Let's make some measurements of an nfet by hooking it up to a couple of voltage sources to generate different values for V_{GS} and V_{DS} :



We've included an ammeter (built from a 0v voltage source) so we can measure I_{DS} , the current flowing through the mosfet from its drain terminal to its source terminal. Here's the translation of the schematic into our netlist format:

```
* plot Ids vs. Vds for 5 different Vgs values
.include "/mit/6.004/jsim/nominal.jsim"
Vmeter vds drain 0v
Vds vds 0 0v
Vgs gate 0 0v
* N-channel mosfet used for our test
M1 drain gate 0 0 NENH W=1.2u L=600n
.dc Vds 0 5 .1 Vgs 0 5 1
.plot I(Vmeter)
```

The first line is a comment. The second line is a control statement that directs JSim to include a netlist file containing the mosfet model parameters for the manufacturing process we'll be targeting this semester. The pathname that's shown will work when running on Athena; if you're running at home you'll need to specify the directory where you downloaded the 6.004 tools. To make your life easier, you may want to copy nominal.jsim and other ".include" files into your Athena directory and use a relative pathname so that you don't have to modify your files when moving them back and forth.

The next three lines specify three voltage sources; each voltage source specifies the two terminal nodes and the voltage we want between them. Note that the reference node for the circuit (marked with a ground symbol in the schematic) is always called "0". The "v" following the voltage specification isn't a legal scale factor and will be ignored by JSim – it's included just remind ourselves that last number is the voltage of the voltage source. All three sources are initially set to 0 volts but the voltage for the Vds and Vgs sources will be changed later when JSim processes the ".dc" control statement.

We can ask JSim to plot the current through voltage sources, which is how we'll see what I_{DS} is for different values of V_{GS} and V_{DS} . We could just ask for the current of the VDS voltage source, but the sign would be wrong since JSim uses the convention that positive current flows from the

2: Characterizing MOSFETs

positive to negative terminal of a voltage source. So we introduce a 0-volt source with its terminals oriented to produce the current sign we're looking for.

The sixth line is the mosfet itself, where we've specified (in order) the names of the drain, gate, source and substrate nodes of the mosfet. The next item names the set of model parameters JSim should use when simulating this device; specify "NENH" to create an nfet and "PENH" for a P-channel mosfet ("pfet"). The final two entries specify the width and length of the mosfet. Note that the dimensions are in microns (1E-6 meters) since we've specified the "u" scale factor as a suffix. **Don't forget the "u" or your mosfets will be meters long!** You can always use scientific notation (e.g., 1.2E-6) if suffixes are confusing.

The seventh line is a control statement requesting a DC analysis of the circuit made with different settings for the Vds and Vgs voltage sources: the voltage of Vds is swept from 0V to 5V in .1V steps, and the voltage of Vgs is swept from 0V to 5V in 1V steps. Altogether 51 * 6 separate measurements will be made.

The eighth and final line requests that JSim plot the current through the voltage source named "Vmeter". JSim knows how to plot the results from the dual voltage sweep requested on the previous line: it will plot I(Vmeter) vs. the voltage of source Vds for each value of voltage of the source Vgs—there will be 6 plots in all, each consisting of 51 connected data points.

After you enter the netlist above, you might want to save your efforts for later use by using the "save file" button. To run the simulation, click the "device-level simulation" button on the tool bar. After a pause, a waveform window will pop up where we can take some measurements. As you move the mouse over the waveform window, a moving cursor will be displayed on the first waveform above the mouse's position and a readout giving the cursor coordinates will appear in the upper left hand corner of the window. To measure the delta between two points, position the mouse so the cursor is on top of the first point. Now click left and drag the mouse (i.e., move the mouse while holding its left button down) to bring up a second cursor that you can then position over the second point. The readout in the upper left corner will show the coordinates for both cursors and the delta between the two coordinates. You can return to one cursor by releasing the left button.

We're now ready to make some measurements:

On-line question 1A:

To get a sense of how well the channel of a turned-on mosfet conducts, let's estimate the effective resistance of the channel while the mosfet is in the linear conduction region. We'll use the $V_{gs} = 5V$ curve (the upper-most plot in the window). The actual effective resistance at any point can be determined from Ohm's Law and is given by $\partial V_{DS} / \partial I_{DS}$, which clearly depends on which V_{DS} we choose. Let's use $V_{DS} = 1.2V$. We could determine the resistance graphically from the slope of a line tangent to the I_{DS} curve at $V_{DS} = 1.2V$. But we can get a rough idea of the channel resistance by determining the inverse of the slope of a line passing through the origin and the point we chose on the I_{DS} curve, i.e., $1.2V / I_{DS}$.

Of course, the channel resistance depends on the dimensions of the mosfet we used to make the measurement. For mosfets, their I_{DS} is proportional to W/L where W is the width of the mosfet (1.2 microns in this example) and L is the length (0.6 microns in this

2: Characterizing MOSFETs

example). When reporting the effective channel resistance, it's useful to report the *sheet resistance*, i.e., the resistance when $W/L = 1$. That way you can easily estimate the effective channel resistance for size device by scaling the sheet resistance appropriately. Since $W/L = 2$ for the device you measured, it conducted twice as much current and has half the channel resistance as a device with $W/L = 1$, so you need to double the channel resistance you computed above in order to estimate the effective channel sheet resistance.

Use the on-line questions page for this lab to report the value for I_{DS} that you measured and the effective channel sheet resistance you calculated from that measurement.

On-line question 1B:

Now let's see how well the mosfet turns "off." Take some measurements of I_{DS} at various points along the $V_{GS}=0V$ curve (the bottom-most plot in the window). Notice that they aren't zero! Mosfets do conduct minute amounts of current even when officially "off", a phenomenon called "subthreshold conduction." While negligible for most purposes, this current is significant if we are trying to store charge on a capacitor for long periods of time (this is what DRAMs try to do). Make a measurement of I_{DS} when $V_{GS}=0V$ and $V_{DS}=2.5V$. Based on this measurement report how long it would take for a .05pF capacitor to discharge from 5V to 2.5V, i.e., to change from a valid logic "1" to a voltage in the forbidden zone. Recall from 6.002 that $Q = CV$, so we can estimate the discharge time as $\Delta t = C(\Delta V / I_{OFF})$. So if our mosfet switch controls access to the storage capacitor, you can see we'll need to refresh the capacitor's charge at fairly frequent intervals.

3: Gate-level timing

The following JSim netlist shows how to define your own circuit elements using the “.subckt” statement:

```
* circuit for Lab#1, parts C thru F
.include "/mit/6.004/jsim/nominal.jsim"

* 2-input NAND: inputs are A and B, output is Z
.subckt nand2 a b z
MPD1 z a 1 0 NENH sw=8 sl=1
MPD2 1 b 0 0 NENH sw=8 sl=1
MPU1 z a vdd vdd PENH sw=8 sl=1
MPU2 z b vdd vdd PENH sw=8 sl=1
.ends

* INVERTER: input is A, output is Z
.subckt inv a z
MPD1 z a 0 0 NENH sw=16 sl=1
MPU1 z a vdd vdd PENH sw=16 sl=1
.ends
```

The “.subckt” statement introduces a new level of netlist. All lines following the “.subckt” up to the matching “.ends” statement will be treated as a self-contained subcircuit. This includes model definitions, nested subcircuit definitions, electrical nodes and circuit elements. The only parts of the subcircuit visible to the outside world are its terminal nodes which are listed following the name of the subcircuit in the “.subckt” statement:

```
.subckt name terminals...
* internal circuit elements are listed here
.ends
```

In the example netlist, two subcircuits are defined: “nand2” which has 3 terminals (named “a”, “b” and “z” inside the nand2 subcircuit) and “inv” which has 2 terminals (named “a” and “z”).

Once the definitions are complete, you can create an instance of a subcircuit using the “X” circuit element:

```
Xid nodes... name
```

where *name* is the name of the circuit definition to be used, *id* is a unique name for this instance of the subcircuit and *nodes...* are the names of electrical nodes that will be hooked up to the terminals of the subcircuit instance. There should be the same number of nodes listed in the “X” statement as there were terminals in the “.subckt” statement that defined *name*. For example, here’s a short netlist that instantiates 3 NAND gates (called “g0”, “g1” and “g2”):

```
Xg0 d0 ct1 z0 nand2
Xg1 d1 ct1 z1 nand2
Xg2 d2 ct1 z2 nand2
```

The node “ct1” connects to all three gates; all the other terminals are connected to different nodes. Note that any nodes that are *private* to the subcircuit definition (i.e., nodes used in the subcircuit

3: Gate-level timing

that don't appear on the terminal list) will be unique for each instantiation of the subcircuit. For example, there is a private node named "1" used inside the nand2 definition. When JSim processes the three "X" statements above, it will make three independent nodes called "xg0.1", "xg1.1" and "xg2.1", one for each of the three instances of nand2. There is no sharing of internal elements or nodes between multiple instances of the same subcircuit.

It is sometimes convenient to define nodes that are shared by the entire circuit, including subcircuits; for example, power supply nodes. The ground node "0" is such a node; all references to "0" anywhere in the netlist refer to the same electrical node. The included netlist file nominal.jsim defines another shared node called "vdd" using the following statements:

```
.global vdd
VDD vdd 0 3.3v
```

The example netlist above uses "vdd" whenever a connection to the power supply is required.

The other new twist introduced in the example netlist is the use of symbolic dimensions for the mosfets ("SW=" and "SL=") instead of physical dimensions ("W=" and "L="). Symbolic dimensions specify multiples of a parameter called SCALE, which is also defined in nominal.jsim:

```
.option SCALE=0.6u
```

So with this scale factor, specifying "SW=8" is equivalent to specifying "W=4.8u." Using symbolic dimensions is encouraged since it makes it easier to determine the W/L ratio for a mosfet (the current through a mosfet is proportional to W/L) and it makes it easy to move the design to a new manufacturing process that uses different dimensions for its mosfets. Note that in almost all instances "SL=1" since increasing the channel length of a mosfet reduces its current carrying capacity, not something we're usually looking to do.

We'll need to keep the PN junctions in the source and drain diffusions reverse biased to ensure that the mosfets stay electrically isolated, so the substrate terminal of nfet (those specifying the "NENH" model) should always be hooked to ground (node "0"). Similarly the substrate terminal of pfet (those specifying the "PENH" model) should always be hooked to the power supply (node "vdd").

With the preliminaries out of the way, we can tackle some design issues:

On-line question 1C:

To maximize noise margins we want to have the transition in the voltage transfer characteristic (VTC) of the nand2 gate centered halfway between ground and the power supply voltage (3.3V). To determine the VTC for nand2, we'll perform a dc analysis to plot the gate's output voltage as a function of the input voltage using the following additional netlist statements:

```
* dc analysis to create VTC
Xtest vin vin vout nand2
Vin vin 0 0v
```

3: Gate-level timing

```
Vol vol 0 0.3v // make measurements easier!
Voh voh 0 3v   // see part (D)

.dc Vin 0 3.3 .005
.plot vin vout voh vol
```

Combine this netlist fragment with the one given at the start of this section and run the simulation. To center the VTC transition, keep the size of the nfet in the nand2 definition as “SW=8 SL=1” and adjust the width of both pfets until the plots for vin and vout intersect at about 1.65 volts. Just try different integral widths (i.e, 9, 10, 11, ...). Report the integral width that comes closest to having the curves intersect at 1.65V.

On-line question 1D:

The *noise immunity* of a gate is the smaller of the low noise margin ($V_{IL} - V_{OL}$) and the high noise margin ($V_{OH} - V_{IH}$). If we specify $V_{OL} = 0.3V$ and $V_{OH} = 3.0V$, what is the largest possible noise immunity we could specify and still have the “improved” NAND gate of part (C) be a legal member of the logic family?

Hint: to measure the low noise margin, use the VTC to determine what V_{IN} has to be in order for V_{OUT} to be 3V, and then subtract V_{OL} (0.3V) from that number. To measure the high noise margin, use the VTC to determine what V_{IN} has to be in order for V_{OUT} to be 0.3V, and then subtract that number from V_{OH} (3.0V). We’ve added some voltage sources corresponding to V_{OL} and V_{OH} to make it easier to make the measurements on the VTC plot.

NOTE: make these measurements using your “improved” nand2 gate that has the centered VTC, i.e., with the updated widths for the PFETS.

Now that we have the mosfets ratioed properly to maximize noise immunity, let’s measure the contamination time (t_c) and propagation time (t_p) of the nand2 gate. The *contamination delay*, t_{CD} , for the nand2 gate will be a lower bound for all the t_c measurements we make. Similarly, the *propagation delay*, t_{PD} , for the nand2 gate will be an upper bound for all the t_p measurements.

Recall that the contamination time is the period of output validity after the inputs have become invalid. So for nand2:

$$\begin{aligned} t_{C-FALL} &= \text{time elapsed from when input} > V_{IL} \text{ to when output} < V_{OH} \\ t_{C-RISE} &= \text{time elapsed from when input} < V_{IH} \text{ to when output} > V_{OL} \\ t_C &= \min(t_{C-RISE}, t_{C-FALL}) \end{aligned}$$

Similarly the propagation time is the period of output invalidity after the inputs have become valid. So for nand2:

$$\begin{aligned} t_{P-RISE} &= \text{time elapsed from when input} \leq V_{IL} \text{ to when output} \geq V_{OH} \\ t_{P-FALL} &= \text{time elapsed from when input} \geq V_{IH} \text{ to when output} \leq V_{OL} \\ t_P &= \max(t_{P-RISE}, t_{P-FALL}) \end{aligned}$$

Following standard practice, we’ll choose the logic thresholds as follows:

3: Gate-level timing

$V_{OL} = 10\%$ of power supply voltage = .3V

$V_{IL} = 20\%$ of power supply voltage = .6V


$V_{IH} = 80\%$ of power supply voltage = 2.6V

$V_{OH} = 90\%$ of power supply voltage = 3V

You can use a voltage source with either a pulse or piece-wise linear waveform to generate test signals for your circuit. Here's how to enter them in your netlist:

```
Vid output 0 pulse(val1 val2 td tr tf pw per)
```

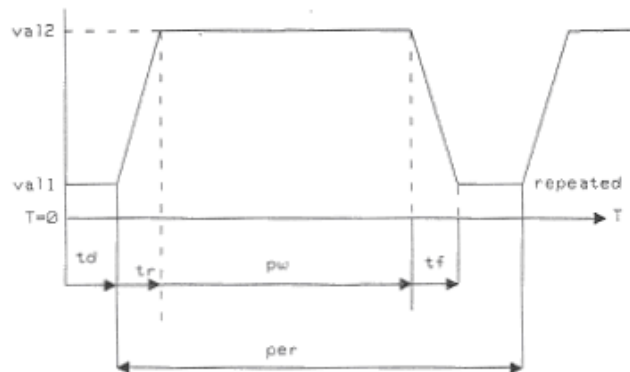This statement produces a periodic waveform with the following shape:



Don't forget to specify your times in nanoseconds (use an "n" suffix)! **Do not specify zero rise and fall times** since the simulation will probably fail to converge. To construct a piece-wise linear waveform, you need to supply a list of time,voltage pairs:

```
Vid output 0 pwl(t1 v1 t2 v2 ... tn vn)
```

The voltage will be v1 for times before t1, and vn for times after tn.

On-line question 1E:

Replace the netlist fragment from (C) with the following test circuit that will let us measure various delays:

```
* test jig for measuring tcd and tpd
Xdriver vin nin inv
Xtest vdd nin nout nand2
Cload nout 0 .02pf
Vin vin 0 pulse(3.3,0,5ns,.1ns,.1ns,4.8ns)

Vol vol 0 0.3v // make measurements easier!
Vil vil 0 0.6v
Vih vih 0 2.6v
Voh voh 0 3.0v

.tran 15ns
.plot vin
```

3: Gate-level timing

```
.plot nin nout vol vil vih voh
```

NOTE: make these measurements using your “improved” nand2 gate that has the centered VTC, i.e., with the updated widths for the pfets.

We use an inverter to drive the nand2 input since we would normally expect the test gate to be driven by the output of another gate (there are some subtle timing effects that we’ll miss if we drive the input directly with a voltage source). Run the simulation and measure the contamination and propagation delays for both the rising and falling output transitions. (You’ll need to zoom in on the transitions in order to make an accurate measurement.) Combine as described above to produce estimates for t_C and t_P .

On-line question 1F:

We mentioned several times in lecture the desire to have our circuits operate reliably over a wide range of environmental conditions. We can have JSim simulate our test circuit at different temperature by adding a “.temp” control statement to the netlist. Normally JSim simulates the circuit at room temperature (25°C), but we can simulate the circuit at, say, 100°C by adding the following to our netlist:

```
.temp 100
```

For many consumer products, designs are tested in the range of 0°C to 100°C. Repeat your measurements of part (E) at 100°C and report your findings. Recompute your estimates for t_C and t_P indicating which measurement(s) determined your final choice for the two delays.

Based on your experiment, if a Pentium 4 processor is rated to run correctly at 3Ghz at 100°C, how fast can you clock it and still have it run correctly at room temperature (assuming t_{PD} is the parameter that determines “correct” behavior)? This is why you can usually get away with overclocking your CPU—it’s been rated for operation under much more severe environmental conditions than you’re probably running it at!

4: CMOS logic-gate design

As the final part of this lab, your mission is to design and test a CMOS circuit that implements the function $F(A,B,C) = C + A \cdot B$ using nfets and pfets. The truth table for F is shown below:

A	B	C	F(A,B,C)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Your circuit must contain no more than 8 mosfets. Remember that **only nfets should be used in pulldown circuits** and **only pfets should be in pullup circuits**. Hint: using six mosfets, implement the complement of F as one large CMOS gate and then use the remaining two mosfets to invert the output of your large gate.


Enter the netlist for F as a subcircuit that can be tested by the test-jig built into lab1checkoff.jsim (a file that we supply and which can be found in the course locker). Note that the checkoff circuitry expects your F subcircuit to have exactly the terminals shown below – the inside circuitry is up to you, but the “.subckt F...” line in your netlist should match exactly the one shown below.

```
.include "/mit/6.004/jsim/nominal.jsim"
.include "/mit/6.004/jsim/lab1checkoff.jsim"

... you can define other subcircuits (eg, INV or NAND gates) here ...

.subckt F A B C Z
... your circuit netlist here
.ends
```

lab1checkoff.jsim contains the necessary circuitry to generate the appropriate input waveforms to test your circuit. It includes a .tran statement to run the simulation for the appropriate length of time and a few .plot statements which will display the input and output waveforms for your circuit.

 For faster simulation, use the  (fast transient analysis) button!

5: Checkoff

When you are satisfied your circuit works, you can start the checkoff process by making sure your top-level netlist is visible in the edit window and that you've complete a successful simulation run. Then click on the green checkmark in the toolbar. JSim proceeds with the following steps:

1. JSim verifies that a .checkoff statement was found when your netlist was read in.
2. JSim processes each of the .verify statements in turn by retrieving the results of the most recent simulation and comparing the computed node values against the supplied expected values. It will report any discrepancies it finds, listing the names of the nodes it was checking, the simulated time at which it was checking the value, the expected value and the actual value.
3. When the verification process is successful, Jsim asks for your 6.004 user name and password (the same ones you use to login to the on-line assignment system) so it can send the results to the on-line assignment server.
4. JSim sends your circuits to the on-line assignment server, which responds with a status message that will be displayed for you. If you've misentered your username or password you can simply click on the green checkmark to try again. Note that the server will check if your circuit has at most 8 mosfets – if it contains more, you'll see a message to that effect and your check-in will not complete.

If you have any difficulties with checkoff, talk to a TA or post a question on Piazza. **Remember to schedule a lab checkoff meeting with a member of the course staff after you complete the on-checkoff and on-line questions. This meeting can happen after the due date of the lab but must be completed within one week of the lab's due date in order to receive full credit.**